



APECE-302: Radio & Television Engineering

Applied Physics, Electronics & Communication Engineering

Lecture # 05



University of
Dhaka | APECE
DU

Course Teacher: Dr. S.M. Riazul Islam

Date: 2012 Year, 05 Month, 10 Day



Contents

- Noise figure
- Calculation of noise figure
- Noise figure in terms of noise resistance
- Noise temperature

Noise Figure and Calculation


❑ Noise Figure

Noise Figure:

$$F = \frac{S/N \text{ at the input}}{S/N \text{ at the output}}$$

- (i) Determine the input signal power S_i
- (ii) Determine the input noise power N_i
- (iii) Calculate the input signal-to-noise power ratio S_i/N_i
- (iv) Determine the output signal power S_o
- (v) Determine the output noise power N_o
- (vi) Calculate the output signal-to-noise power ratio S_o/N_o
- (vii) From steps (iii) and (vi) calculate the noise figure F .

❑ Calculation of Noise Figure

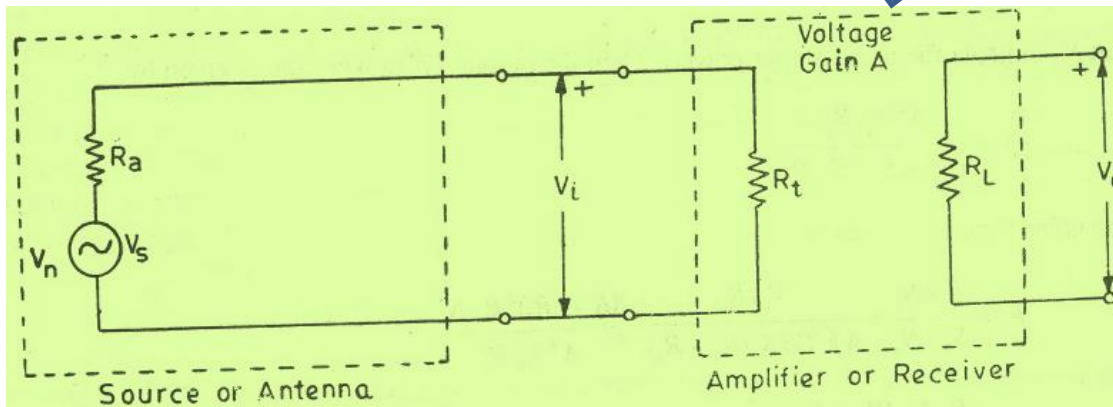

$$V_{si} = \frac{V_s R_t}{R_a + R_t}$$

$$S_i = \frac{V_{si}^2}{R_t} = \left(\frac{V_s \cdot R_t}{R_a + R_t} \right)^2 \frac{1}{R_t} = \frac{V_s^2 R_t}{(R_a + R_t)^2}$$

Calculation of Noise Figure

Input noise voltage is given by,

$$V_{ni}^2 = 4 \bar{k} T B \frac{R_a R_i}{R_a + R_i}$$

Hence input noise power is,

$$N_i = \frac{V_{ni}^2}{R_i} = \frac{4 \bar{k} T B R_a}{R_a + R_i}$$

The input signal-to-noise power ratio is given by,

$$\frac{S_i}{N_i} = \frac{V_s^2 R_i}{(R_a + R_i)^2} \cdot \frac{(R_a + R_i)}{4 \bar{k} T B R_a} = \frac{V_s^2 R_i}{4 \bar{k} T B R_a (R_a + R_i)}$$

The output signal power is given by,

$$\begin{aligned} S_o &= \frac{V_{so}^2}{R_L} = \frac{(A V_{si})^2}{R_L} = \left(\frac{A V_s R_i}{R_a + R_i} \right)^2 \cdot \frac{1}{R_L} \\ &= \frac{A^2 V_s^2 R_i^2}{(R_a + R_i)^2 R_L} \end{aligned}$$

Calculation of Noise Figure

$$\frac{S_o}{N_o} = \frac{A^2 V_s^2 R_i^2}{(R_a + R_i)^2 R_L N_o}$$

Hence the noise figure is given by,

$$F = \frac{S_i / N_i}{S_o / N_o} = \frac{V_s^2 R_i}{4 \bar{k} T B R_a (R_a + R_i)} \cdot \frac{(R_a + R_i)^2 R_L N_o}{A^2 V_s^2 R_i^2}$$

$$= \frac{R_L N_o (R_a + R_i)}{4 \bar{k} T B A^2 R_a T_i}$$

Noise Figure in terms of Noise Resistance

Equivalent noise resistance

$$R_{eq} = R_1 + R_2' = R_1 + \frac{R_2}{A_1^2} + \frac{R_3}{A_1^2 A_2^2}$$

I/P resistance of the first stage

Eq. noise resistance of the first stage

Noise resistance of the subsequent stages referred to the I/P of the first stage

$$R_{eq}' = R_{eq} - R_i$$

$$R = R_{eq}' + \frac{R_a R_i}{R_a + R_i}$$

$$V_{ni} = \sqrt{4 \bar{k} T B R}$$

Noise Figure in terms of Noise Resistance

Substitute N_o

$$N_o = \frac{V_{no}^2}{R_L} = \frac{(A V_{ni})^2}{R_L} = \frac{A^2 4 \bar{k} T B R}{R_L}$$

$$F = \frac{R_L (R_a + R_t)}{4 \bar{k} T B A^2 R_a R_t} \cdot \frac{A^2 4 \bar{k} T B R}{R_L}$$

$$= R \frac{R_a + R_t}{R_a R_t} = \left(R_{eq}' + \frac{R_a R_t}{R_a + R_t} \right) \cdot \frac{R_a + R_t}{R_a R_t} = 1 + R_{eq}' \frac{R_a + R_t}{R_a \cdot R_t}$$

$R_t \gg R_a$

$$F = 1 + \frac{R_{eq}'}{R_a}$$

Noise Temperature

- ❑ Noise Figure is a good indicator of noise performance
 - ❑ However, UHF, microwave low noise antenna, Rx or devices!
 - ❑ Noise temp \ll addition of noise power from several sources

$$P_i = \bar{k} T_i B$$

$$P_i = P_1 + P_2 = \bar{k} B T_1 + \bar{k} B T_2$$

$$\bar{k} B T_i = \bar{k} B (T_1 + T_2)$$

$$T_i = T_1 + T_2$$

Greater variation than F

where P_1 and P_2 are the two individual noise powers which may respectively be the noise powers received by the antenna and the power generated by the antenna.
 T_1 and T_2 are the individual noise temperatures corresponding to P_1 and P_2 respectively and T_i is the total noise temperature.

Noise Temperature

- We introduce equivalent noise temperature, T_{eq} , like Eq. noise resistance

$$F = 1 + \frac{R_{eq}'}{R_a} = 1 + \frac{\bar{k} T_{eq} BR_{eq}'}{\bar{k} T_o BR_a} = 1 + \frac{T_{eq}}{T_o}$$

where

$$R_{eq}' = R_a \text{ as assumed in the definition of } T_{eq},$$

$$T = 27^\circ\text{C} = 300^\circ\text{K}$$

T_{eq} = equivalent noise temperature of the receiver or amplifier under consideration.




Hence

$$T_o F = T_o + T_{eq}$$

$$T_{eq} = T_o (F - 1)$$

Noise Temperature


 A receiver having equivalent noise resistance of 2500Ω and input resistance of 500Ω is connected to an antenna of resistance 50Ω . Compute the noise figure (in dBs) and equivalent noise temperature for the receiver.

Solution.

$$F = 1 + \frac{R_{eq}'}{R_a}$$

$$R_{eq}' = R_{eq} - R_i = 2500 - 500 = 2000 \Omega$$

Hence

$$F = 1 + \frac{2000}{50} = 41$$

$$F \text{ in dB} = 10 \log_{10} 41 = 16.12 \text{ dB}$$

$$T_{eq} = T_o (F - 1) = 300 (41 - 1) = 1200^\circ\text{K.}$$

Q & A

